


# ECE 526L

# Lab2
 
## Part-A

In this portion of the Lab, first design a half adder and named half\_adder.v

For a half adder you need to implement on gate level by using one xor and one and gate.



```
module half_adder(  
    input a,      // Input 'a'  
    input b,      // Input 'b'  
    output s,     // Output 's' (Sum)  
    output c      // Output 'c' (Carry)  
);  
.  
.  
.  
  
endmodule
```

//////////////////////////////////TB

Then write test bench that covers all inputs values and name the module as half\_adder\_tb.v

Then use the command


```
vcs -debug_access+all half_adder.v half_adder_tb.v
```

Simulate the code and cover all cases to test all possible combinations of and print out all test cases on consol.

Inputs		Outputs	
A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
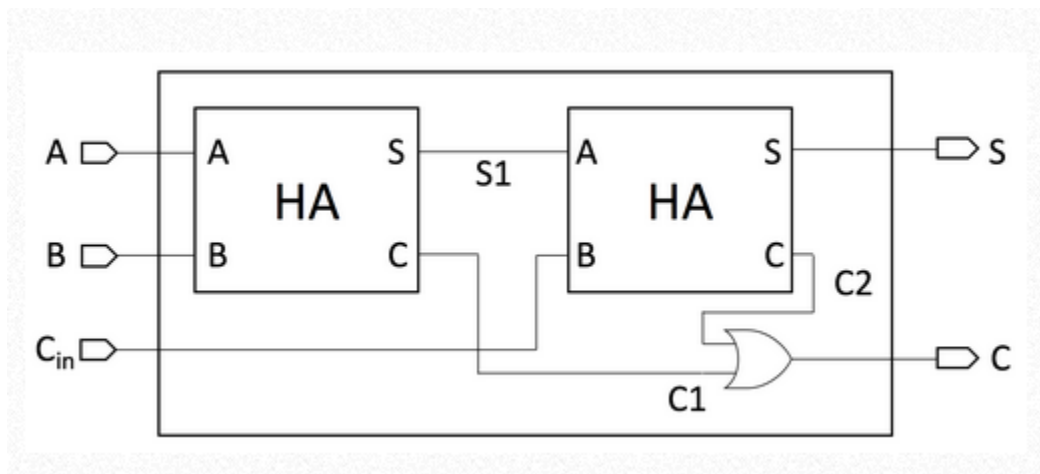
## Part-B

In this part we will use the half adder from Part-A to make a full adder.(by instantiation of half\_adder) and name it full\_adder.v



To make a full adder we will use 2 half adders and a OR primitive

Then write test bench that covers all inputs values and name the module as full\_adder\_tb.v

Then use the command

```
vcs -debug_access+all half_adder.v full_adder.v full_adder_tb.v
```

Simulate the code and cover all cases to test all possible combinations of and print out all test cases on consol.

a	b	Cin	Sum	cout	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	
1	0	0	0	1	
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	

```

module full_adder(
    A, //input A
    B, //input B
    C, //input C
    Sum,
    Carry_out
);
    input A;
    input B;
    input C;
    output Sum;
    output Carry_out;

```

-----TB-----

```

module tb_full_adder;

    // Inputs
    reg Data_in_A;
    reg Data_in_B;
    reg Data_in_C;

    // Outputs
    wire Data_out_Sum;
    wire Data_out_Carry;

```

```
// Instantiate the Unit Under Test (UUT)  
full_adder uut (
```

```
end module;
```